

# University of KwaZulu-Natal

## Electrical, Electronic & Computer Engineering

Examinations: June 2026

Subject, Course & Code: Electrical Principles 1 ENEL2EA

Duration: 3 Hours

Total Marks: 100

### Examiner/s:

S Rezenom (Internal)  
N Sibanda (Internal)  
Prof T Quazi (Moderator)

### Instructions:

1. This paper consists of “**Section A**” and “**Section B**”. Use **separate answer sheets** for each section.
2. Clearly label the answer sheets as “**Section A**” or “**Section B**” to provide clarity.
3. **Section A** consists of **three questions**. All questions must be answered in full. All relevant assumptions must be documented clearly.
4. **Section B** consists of **two questions**. All questions must be answered in full. All relevant assumptions must be documented clearly.
5. A dark pencil may be used.

## ENEL2EA SECTION A

### Question 1A Mesh and Thevenin's Theorem [15 marks]

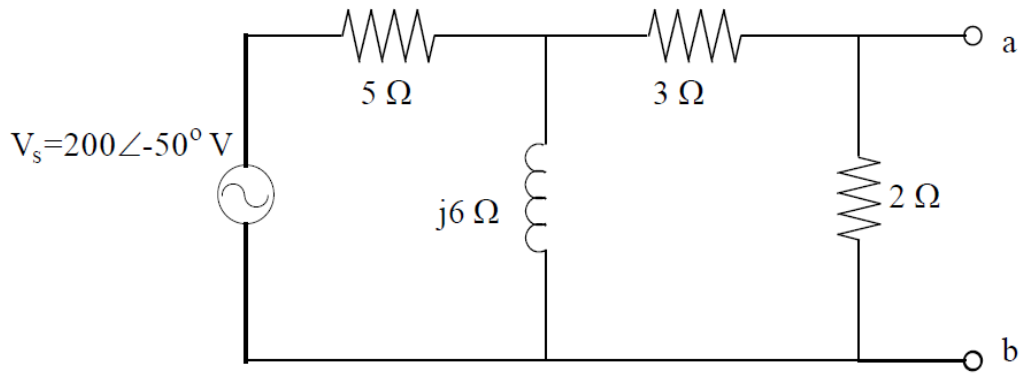


Figure Q1A.

For the circuit shown in Figure Q1A above:

- Using Kirchoff's voltage laws, determine the expression for the loop currents. [2]
- Solve for the loop currents. [5]
- Determine the Thevenin voltage. [2]
- Solve for the Thevenin impedance. [4]
- If maximum power is to be transferred to a load  $Z_L$  at a-b terminals, determine  $Z_L$  and the power transferred to the load. [2]

### Question 2A Nodal and Nortons Theorem [15 marks]

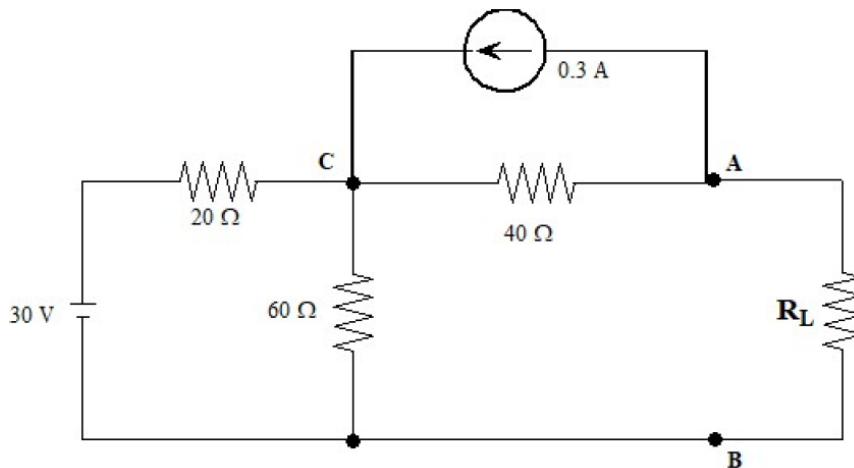


Figure Q2A.

- a) Using Nodal analysis, determine the Norton equivalent of the circuit in Figure Q2A. (In other words, find  $I_N$  of the circuit in Figure Q2A, assuming the load will be connected between A and B. Also, find  $R_N$  of the circuit in Figure Q2A, assuming the load will be connected between A and B. Finally, draw the equivalent circuit). [13]
- b) Determine the value of  $R_L$  that results in maximum power transfer, and the actual power delivered to the load. [2]

### Question 3A RLC Circuits [20 marks]

For the network in Figure Q3A:

- a) Determine the mathematical expression for the inductor current following the closure of the switch S at time  $t=0$  onto position 1. [5]
- b) Determine the inductor voltage and current at  $t = 0$  and  $t = 100$  milliseconds. [6]
- c) If the switch is closed onto position 2 when  $t = 100$  milliseconds, determine the new expression for the inductor current, and the voltage across resistor R. [5]
- d) Plot the inductor current waveform from  $t = 0$  to  $t = 200$  milliseconds. [4]

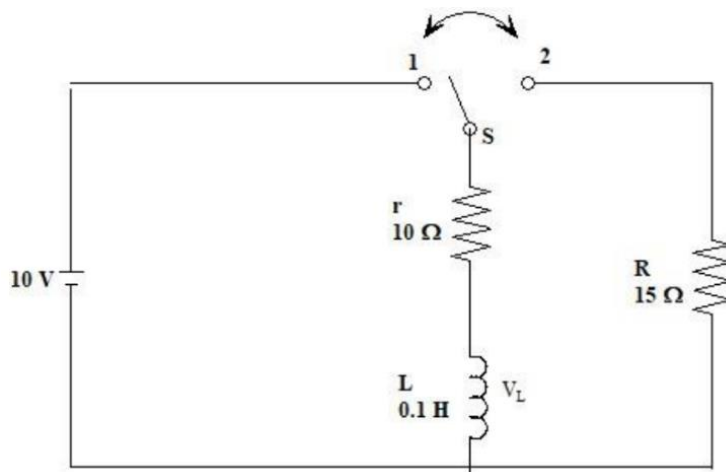


Figure Q3A.

## ENEL2EA SECTION B

### Question 1B [25 marks]

- a) Consider the circuit shown in Figure Q1B. Three loads are connected in parallel across a 250 V (rms) voltage source  $V_s$ .

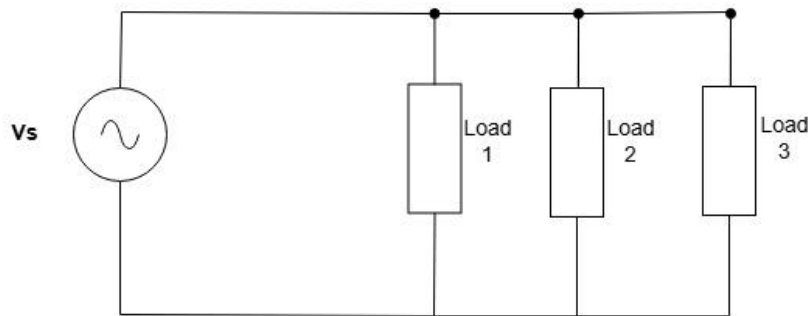


Figure Q1B.

*Load 1* absorbs 30 kVA at power factor of 0.8 leading.

*Load 2* absorbs 20 kVA at power factor of 0.6 lagging.

*Load 3* absorbs 6 kW at unity power factor.

- i) Clearly plot the power diagrams for each of the three loads. [3]
  - ii) Compute the power factor of the equivalent load. [2]
  - iii) Compute the value of the reactance that would be connected across the loads that brings the power factor of the loads to 0.9 leading. [5]
- b) A three-phase Y-connected generator is connected to a three-phase Y-connected load. Assume the phase voltage is 220 V (rms) at  $0^\circ$  at *phase a* of the generator. Assume positive phase sequence (*abc* phase sequence). The balanced load consists of  $100 + j 200 \Omega$  impedances. Compute
- i) the line voltages  $V_{ab}$ ,  $V_{bc}$ , and  $V_{ca}$ . [3]
  - ii) line currents  $I_a$ ,  $I_b$ , and  $I_c$ . [3]
- c) The line voltage (magnitude in rms) at the terminals of a balanced Y-connected load is 6600 V. The load impedance is  $200 + j 60 \Omega$ . Assume the line connecting the voltage source to the load has an impedance of  $0.5 + j 4.0 \Omega$ .
- i) Compute the magnitude of the line current. [3]
  - ii) Compute the magnitude of the line voltage at the source. [3]
- d) Briefly explain the significance of power factor correction in the context of power generation and distribution systems. [3]

**Question 2B [25 marks]**

- a) Consider the magnetic circuit shown in Figure Q2B that is made of sheet steel with relative permeability of 6000. A coil of 500 turns coil is applied at the sections between points *b-e*. All sections have an area ( $A_c$ ) of  $5.0 \text{ cm}^2$ . The length between the points shown is  $20.0 \text{ cm}$ , except for the right leg of the system which has an air gap of  $2.0 \text{ mm}$ . Assume there is no fringing in the air gap. Calculate the value of current that causes a flux in the gap of  $2 \times 10^{-4} \text{ Wb}$ . [10]

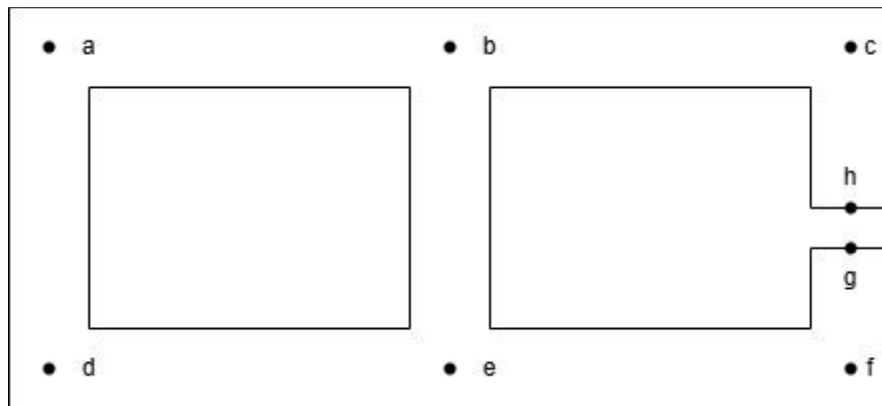


Figure Q2B.

- b) A 23 kVA, 2300/230-V, 60-Hz, step-down transformer has the following parameters ( $\Omega$ ):

$$\begin{array}{ll} R_1 = 1.2 & X_1 = 3.0 \\ R_2 = 0.012 & X_2 = 0.03 \\ R_c = 2000 & X_m = 1800 \end{array}$$

Assume the transformer is operating at 80% of its load at rated terminal voltage and 0.6 pf lagging. Compute the efficiency of the transformer. [6]

- c) Briefly explain the concept of eddy currents in transformers and describe how its effect is reduced. [4]
- d) A series DC generator supplies 200 V at 40 A to a load. The resistance of the series field is  $10 \Omega$  and that of the armature is  $0.06 \Omega$ . Calculate the generated voltage. [5]