

University of KwaZulu-Natal

Electrical, Electronic & Computer Engineering

Examinations: June 2026

Subject, Course & Code: Electrical & Electronic Engineering ENEL2EE

Duration: 3 Hours

Total Marks: 100

Examiner/s:

S Rezenom (Internal)
P Kumar (Internal)
R Khuboni (Moderator)

Instructions:


1. This paper consists of **electrical section** and **electronic section**. Use **separate answer sheets** for each section.
2. Clearly label the answer sheets as “**EC Section**” or “**EL Section**” to provide clarity.
3. The electronic section consists of **two questions**. All questions must be answered in full. All relevant assumptions must be documented clearly.
4. The electrical section consists of **two questions**. All questions must be answered in full. All relevant assumptions must be documented clearly.
5. A dark pencil may be used.

Electronic Section


EC Question 1 [25 marks]

- a) Consider the circuit shown below and determine the operation region of the transistor. The relevant values are $V_B = 5.0\text{ V}$, $V_{CC} = 10\text{ V}$, $V_{BE} = 0.7\text{ V}$, $R_B = 20\text{ k Ohm}$, $R_C = 10\text{ k Ohm}$ and $\beta = 300$.

[5]

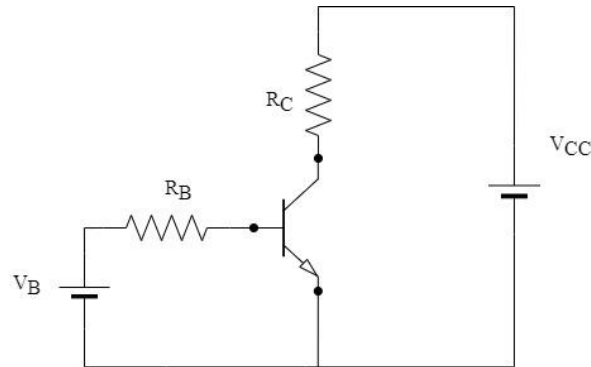


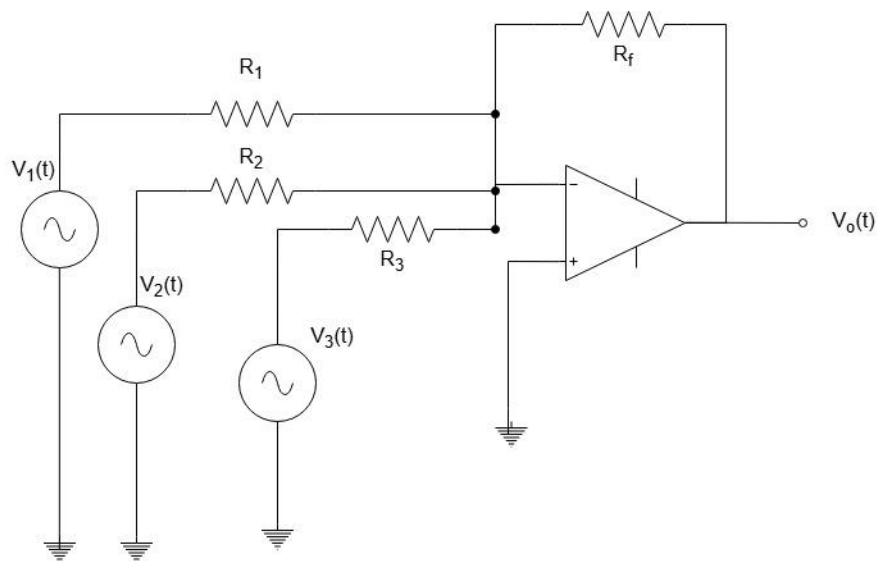- b) Consider the ideal operational amplifier shown below.




- i. Obtain an expression for the output voltage $V_o(t)$ using first principles. [3]
- ii. Assume the input voltages are $V_1(t) = 10 \sin(1000\pi t)$, mV, $V_2(t) = 20 \sin(1000\pi t)$, mV and $V_3(t) = 10 \sin(1000\pi t)$, mV. The resistor values are $R_1 = 10\text{ k Ohm}$, $R_2 = 10\text{ k Ohm}$, $R_3 = 20\text{ k Ohm}$, $R_f = 50\text{ k Ohm}$. Plot the output voltage $V_o(t)$. [2]

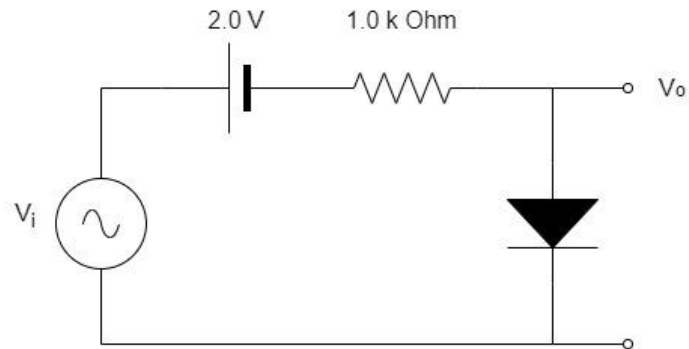- c) Briefly show the equivalent circuit diagram of the non-ideal operational amplifier and explain the relevant parameters. [5]
- d) Consider the circuit shown below. The input voltage is $V_i(t) = 12 \sin(5000\pi t)$, Volts. Assume the threshold voltage of the diode is 1.0 V. Plot the output voltage V_o versus the input voltage V_i . [5]




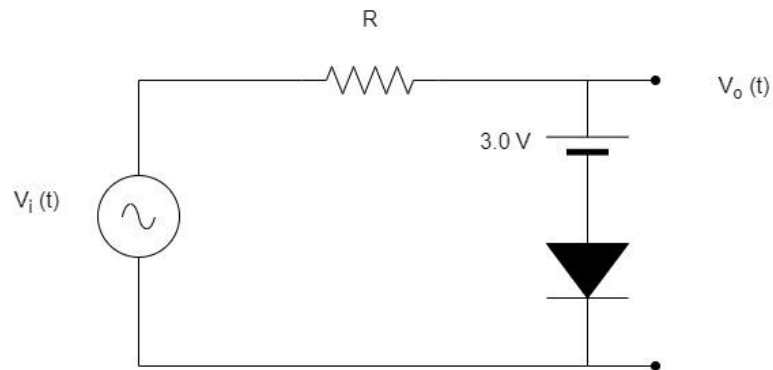- e) The input voltage $V_i(t)$ of the circuit shown below varies from -10 V to 10 V. Plot the current in the resistor. Assume ideal diodes and $R = 1 \text{ k Ohm}$. [5]



EC Question 2 [25 marks]

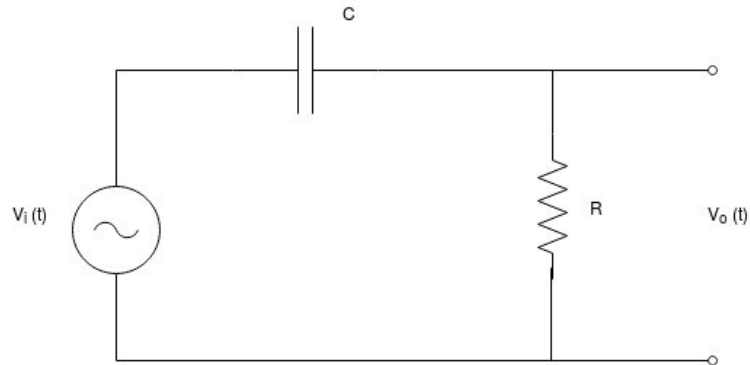- a) Design an operational amplifier that has a gain $-20 \pm 10\%$. Assume 2 % tolerance resistors are available. Clearly document any assumptions. [5]
- b) Consider the circuit shown below.



- i) Derive the transfer function. [5]
- ii) Sketch the approximate plot of the magnitude and phase response. [5]
- c) Consider the Boolean expression $Y = ABC + (AC + \bar{C})(A\bar{B} + BC)$.
- i) Simplify the expression. [5]
- ii) Show the logical circuit of the simplified expression using NAND gates. [5]

Electrical (EL) Section

Question EL1 [30 marks]:

- (a) Using nodal voltage analysis, determine the voltages V_1 , V_2 and V_3 in the circuit of Fig. QEL1(a). [6]

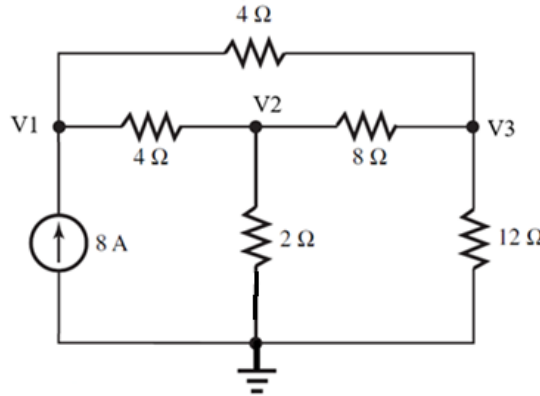


Fig. QEL1(a)

- (b) In Fig QEL1(b), the switch was closed for a long time. The switch is opened at $t=0$ as shown in figure. Determine the voltage across capacitor (v_C) at $t=2$ s. [6]

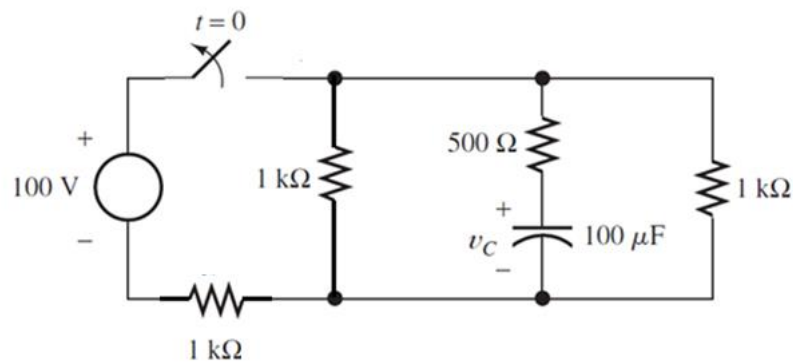


Fig. QEL1(b)

- (c) In the circuit of Fig. QEL1(c), determine the following:
- The mesh current equations for I_1 and I_2 . [2]
 - The Norton's equivalent circuit across the $50\angle -10^\circ \Omega$ impedance. [5]
 - The current (in polar form) in the $50\angle -10^\circ \Omega$ impedance using Norton's equivalent circuit. [2]

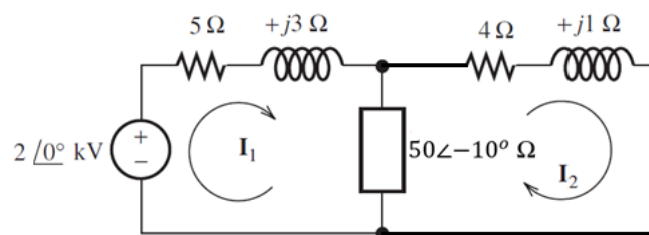


Fig. QEL1(c)

- (d) A balanced three-phase star connected load is connected to a balanced three-phase star connected 50 Hz supply with 400 V between the lines. Each phase of the load consists of a resistance of $20\ \Omega$ and an inductance of 0.05 H connected in series. Determine the following:
- (i) The phase voltages (in polar form). [2]
 - (ii) The magnitude and phase of the load impedance. [3]
 - (iii) The total power supplied to the load. [4]

Question EL2 [20 marks]:

- (a) A 5 kVA, 200/800 V, 50 Hz transformer gave the following test results:
 Open Circuit Test: 2000 V, 1.2 A, 90 W
 Short Circuit Test: 50 V, 5 A, 110 W
 For the open circuit test, the high voltage side was open and for the short circuit test the low voltage side was shorted.
- (i) Calculate the equivalent circuit parameters referred to the low voltage side. [9]
 - (ii) Determine the voltage regulation at full load with 0.7 power factor lagging. [5]
- (b) A self-excited series dc motor takes 40 A at 220 V and runs at 700 rpm. If the armature resistance and field resistance are $0.2\ \Omega$ and $0.1\ \Omega$, respectively, and the rotational losses are 0.4 kW, find:
- (i) The torque developed in the armature, [3]
 - (ii) The output power of the motor. [3]