

University of KwaZulu-Natal
Electrical, Electronic & Computer Engineering Discipline
Main Examination: May/June 2026

DURATION: 2 HOURExaminers: Dr. R. Tiako
Dr F. Khan**TOTAL MARKS: 60**(Internal)
(External)Instructions: Answer all for Parts A & C plus B-1 and any 2 as indicated in Part B

Part A: choose and write the most appropriate answer**[5 Marks]**

1. Identify the characteristic to which the open-circuit characteristic (OCC) of a DC generator corresponds.
[magnetic; internal; external; performance]
2. An industrial process requires smooth and specific variation of motor speed over a wide range. Based on this requirement, select the most suitable reason for using a DC motor
[are inexpensive; have simple construction; provide precise speed control]
3. Determine the effect of adding a controller resistance in series with the armature of a DC motor on its speed.
[only above the normal speed; only below the normal speed; both above and below the normal speed]
4. Identify which currents produce the rotating magnetic field that determines the synchronous speed in an induction motor.
[rotor currents; stator currents; both rotor and stator currents]
5. Identify the factor that determines the copper saving when a two-winding transformer is converted into an autotransformer.
[voltage transformation ratio; secondary load; magnetic properties of the core; size of the core]
6. Classify the type of power conversion performed by a DC chopper.
[AC to DC; AC to AC; DC to DC; DC to AC]

(0.84) X 6 = [5]

Part B: answer B-1 and any other 2 questions**[40 Marks]**

1. A 30 kVA, three-phase step-down transformer (400/120 volt, Y/ Δ -connected) has the following per-phase parameters: primary resistance = 50 m Ω , primary reactance = 100 m Ω , secondary resistance = 12 m Ω , and secondary reactance = 30 m Ω . The core loss resistance is 400 Ω and the magnetizing reactance is 250 Ω . The transformer supplies its rated load at a power factor of 0.8 lagging with a rated secondary voltage of 120 V.

(a) Draw an annotated per phase approximate model of the three-phase transformer. **[5]**

(b) Using 12 kVA as the base power, 60 V as the base voltage on the secondary side, and using the approximate per-phase equivalent circuit of the transformer, draw the per unit circuit of the transformer and determine its per unit input voltage. **[10]**

2. A standard two-winding step-down transformer is reconfigured to operate as a step-up autotransformer. The autotransformer has a rated apparent power of 90 kVA, with a converted power of 72 kVA and a primary current of 750 A.

Determine the nominal primary and secondary voltages of the original two-winding transformer. **[12.5]**

3. A 12 KW shunt generator having an armature circuit resistance of 0.85 Ω and a field resistance of 140 Ω , generates a terminal voltage of 360 V at full load. Determine the developed power at half load condition, assuming the iron, friction and windage losses amount to 700 W. **[12.5]**

4. A DC series motor operates at a speed of 1200 rpm when supplied with a voltage of 500 V and drawing a current of 30 A. The armature resistance is 0.9 Ω , and the series field resistance is 0.5 Ω . Determine the value of an additional resistance that must be connected in series with the motor in order to reduce the speed to 750 rpm, assuming the current remains constant. **[12.5]**

Part C:**[15 Marks]**

A 480 V, 60 Hz, 47 hp, three-phase induction motor draws 60 A at a power factor of 0.85 (lagging). The stator copper losses are 3.5 kW, and the core losses are 2.8 kW. Stray losses may be neglected.

At full-load operation, the motor runs with a slip of 0.02

(a) Determine the friction and windage losses under these full-load conditions. **[12]**

(b) Find the resistance of the stator winding under the condition indicated in (a). **[3]**